

For More Questions [Click Here](#)

**1. When negative voltage feedback is applied to an amplifier, its voltage gain .....**

1. Is increased
- 2. Is reduced**
3. Remains the same
4. None of the above

**2. The value of negative feedback fraction is always .....**

- 1. Less than 1**
2. More than 1
3. Equal to 1
4. None of the above

**3. If the output of an amplifier is 10 V and 100 mV from the output is fed back to the input, then feedback fraction is .....**

1. 10
2. 1
- 3. 01**
4. 15

**4. The gain of an amplifier without feedback is 100 db. If a negative feedback of 3 db is applied, the gain of the amplifier will become .....**

1. 5 db
2. 300 db
3. 103 db
- 4. 97 db**

**5. If the feedback fraction of an amplifier is 0.01, then voltage gain with negative feedback is approximately.....**

1. 500
- 2. 100**
3. 1000
4. 5000

**6. A feedback circuit usually employs ..... network**

- 1. Resistive**
2. Capacitive
3. Inductive
4. None of the above

**7. The gain of an amplifier with feedback is known as ..... gain**

1. Resonant
2. Open loop
- 3. Closed loop**
4. None of the above

**8. When voltage feedback (negative) is applied to an amplifier, its input impedance**

.....

1. Is decreased
- 2. Is increased**
3. Remains the same
4. None of the above

**9. When current feedback (negative) is applied to an amplifier, its input impedance**

.....

- 1. Is decreased**
2. Is increased
3. Remains the same
4. None of the above

**10. Negative feedback is employed in .....**

1. Oscillators
2. Rectifiers
- 3. Amplifiers**
4. None of the above