

For More Questions [Click Here](#)

1. The statement which correctly represents Ohm's law:

1. $V = IR$
 2. $V = R/I$
 3. $R = VI$
 4. $I = R/V$
- Correct answer: 1. $V = IR$

2. A 10 ohms resistor is powered by a 5-V battery. The current flowing through the source is:

1. 10 A
 2. 50 A
 3. 2 A
 4. 0.5 A
- Correct answer: 4. 2 A
○ Solution: From $I = V/R = 5\text{-V}/10\text{ ohm} = 0.5\text{ A}$

3. If $V = 50\text{ V}$ and $I = 5\text{ A}$, then $R = \underline{\hspace{1cm}}$:

1. $50\ \Omega$
 2. $5\ \Omega$
 3. $10\ \Omega$
 4. $2\ \Omega$
- Correct answer: 3. $10\ \Omega$
○ Solution: From $R = V/I = 50\text{ V}/5\text{A} = 10\ \Omega$

4. If $P = 50\text{ watt}$ and $R = 2\text{ ohms}$, then $I = \underline{\hspace{1cm}}?$

1. 50 A
 2. 5 A
 3. 10 A
 4. 2 A
- Correct answer: 3. 5 A
○ Solution: From $I = \sqrt{(P/R)} = \sqrt{(50\text{ V}/2\text{A})} = \sqrt{25}\text{ A} = 5\text{ A}$

5. Unit of voltage is:

1. Volt
 2. Watt
 3. Coulomb
 4. Ampere
1. Correct answer: 1. Volt

6. Unit of current is:

1. Volt
2. Watt
3. Coulomb

4. Ampere

1. Correct answer: 4. Ampere

7. Unit of power is:

1. Volt
2. Watt
3. Coulomb
4. Ampere

1. Correct answer: 2. Watt

8. Unit of resistance is:

1. Volt
2. Watt
3. Ohms
4. Ampere

- o Correct answer: 3. Ohms

9. If $V = 10 \text{ V}$ and $R = 15 \text{ k}\Omega$, then $I = \underline{\hspace{1cm}}$?

1. 0.666 mA
2. 666 μA
3. 0.66 A
4. a & b

- o Correct answer: 4. a & b

- o Solution: Here $I = V/R = 10 \text{ V} / 15 \text{ k}\Omega = 0.666 \text{ mA} = 666 \mu\text{A}$

10. If $I = 5 \text{ A}$ and $R = 10 \Omega$, then $P = \underline{\hspace{1cm}}$?

1. 50 watts
2. 250 watts
3. 350 watts
4. 500 watts

- o Correct answer: 2. 250 watt

- o Solution: Here $P = I^2R = (5 \text{ A})^2 * 10 \Omega = 250 \text{ watts}$