

For More Questions [Click Here](#)

1. In a split phase motor, the running winding should have

- (a) high resistance and low inductance
- (b) low resistance and high inductance
- (c) high resistance as well as high inductance
- (d) low resistance as well as low inductance

Ans: b

2. If the capacitor of a single-phase motor is short-circuited

- (a) the motor will not start
- (b) the motor will run
- (c) the motor will run in reverse direction
- (d) the motor will run in the same direction at reduced r.p.m.

Ans: a

3. In capacitor start single-phase motors

- (a) current in the starting winding leads the voltage
- (b) current in the starting winding lags the voltage
- (c) current in the starting winding is in phase with voltage in running winding
- (d) none of the above

Ans: a

4. In a capacitor start and run motors the function of the running capacitor in series with the auxiliary winding is to

- (a) improve power factor
- (b) increase overload capacity
- (c) reduce fluctuations in torque
- (d) to improve torque

Ans: a

5. In a capacitor start motor, the phase displacement between starting and running winding can be nearly

- (a) 10°
- (b) 30°
- (c) 60°
- (d) 90°

Ans: d

6. In a split phase motor

- (a) the starting winding is connected through a centrifugal switch
- (b) the running winding is connected through a centrifugal switch
- (c) both starting and running windings are connected through a centrifugal switch
- (d) centrifugal switch is used to control supply voltage

Ans: a

7. The rotor developed by a single-phase motor at starting is

- (a) more than i.he rated torque
- (b) rated torque

- (c) less than the rated torque
- (d) zero

Ans: d

8. Which of the following motor will give relatively high starting torque ?

- (a) Capacitor start motor
- (b) Capacitor run motor
- (c) Split phase motor
- (d) Shaded pole motor

Ans: a

9. Which of the following motor will have relatively higher power factor ?

- (a) Capacitor run motor
- (b) Shaded pole motor
- (c) Capacitor start motor
- (d) Split phase motor

Ans: a

10. In a shaded pole motor, the shading coil usually consist of

- (a) a single turn of heavy wire which is in parallel with running winding
- (b) a single turn of heavy copper wire which is short-circuited and carries only induced current
- (c) a multilayer fine gauge copper wire in parallel with running winding
- (d) none of the above

Ans: b